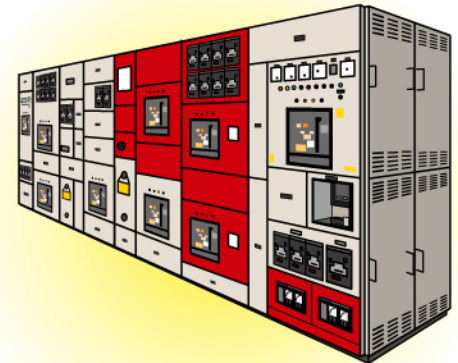


# Case Study:

## Ideal LV Changeover Scheme Design Prevents Building Supply Interruption

### Introduction

LV changeover scheme (LVCOS) is an essential design for maintaining power supply in buildings. In the event of a supply interruption, the scheme will switch to standby supply in order to maintain essential equipment operation. However, if the scheme is susceptible to voltage dips, it may mal-operate leading to an unnecessary changeover. In a worst-case scenario, the whole building may lose supply.




LV Panels in Switch Room
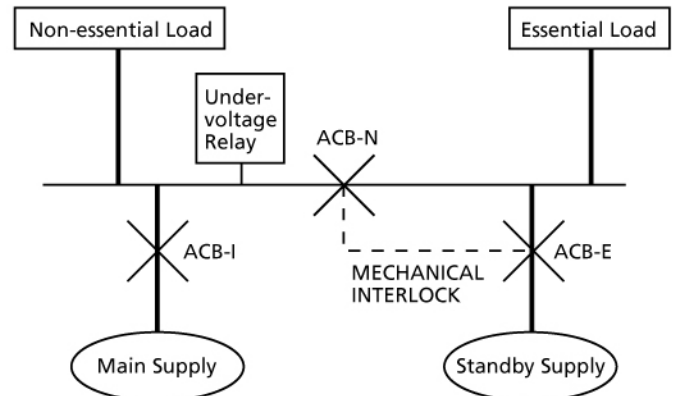
### Case Study

In a voltage dip incident reported recently, building A lost its entire building supply. Air circuit breaker ACB-1 tripped while the standby supply was not activated. To restore electricity supply, manual reset of the entire scheme was required. Restoring the building supply took around half an hour.


In investigating the above case, it was found that the tripping command for ACB-1 was initiated by two main control components. Here were the findings:



Typical LV Changeover Scheme Diagram
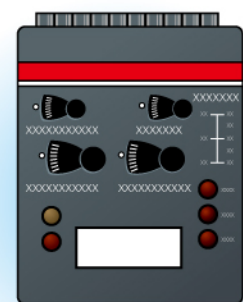
#### 1. 3-ph Under-voltage Relay (UR) - Set at 80%, 2 sec


- UR was designed to power-up by L1-ph
- It was susceptible to voltage dips
- It would operate when L1-ph voltage dipped to 80% remaining for 0.1 sec



3-ph UR
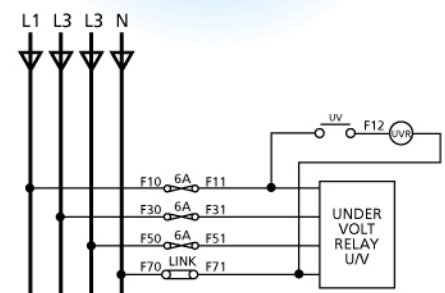
#### 2. Under-voltage Repeat Relay (UVR)

- UVR was supplied by L1-ph
- It was susceptible to voltage dips
- It would drop off when L1-ph voltage dipped to 40% remaining for 0.05 sec



UVR in Wiring Diagram

### 3. Control Components Voltage Dip Ride-through Capability Comparison

After studying the control components, including UVR, contactors, relays, UR and timers, we have summarized their voltage dip ride-through capabilities as shown in the table on the left.


According to the test results, UVR, UR, contactors and relays are more voltage-sensitive, while the timer is more time-sensitive if set with a very short time delay setting.

More Voltage-Sensitive ↑ ↓ Less Voltage-Sensitive	UVR, Contactor, Relay	UR
	Timer with longer time delay setting	Timer with very short time delay setting
	← Less Time-Sensitive	More Time-Sensitive →


As both UR and UVR were susceptible to voltage dip, such that ACB-1 was falsely tripped. On the other hand, the standby supply would not be activated due to voltage dip. Therefore, the whole building lost its supply and manual reset for the scheme was required.

### Recommendations

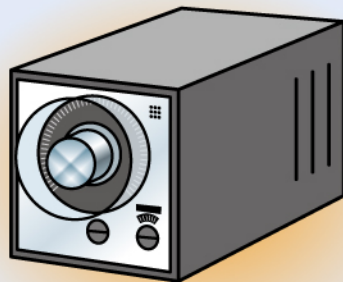1. To employ a UR with good voltage dip ride-through capability or to add a true-off delay timer (TODT) to avoid mal-operation of the UR during voltage dips.
2. To replace the UVR with a DC relay and relocate it to the DC control circuit as shown in the wiring diagram below.



True-off Delay Timer(TODT)

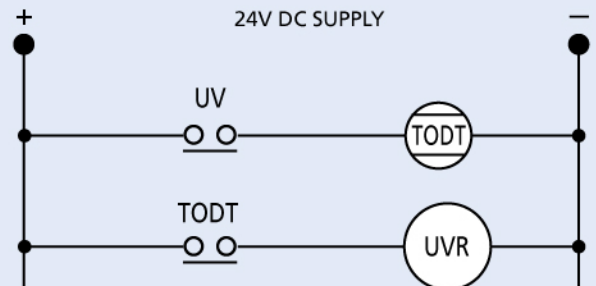

DC Control Circuit with TODT and UVR

### Tips for an Ideal LVCOS Design

1. Use of DC scheme and equipping with battery and charger.
2. If AC control supply has to be installed, it should be protected by batteryless UPS.
3. To employ UR with good voltage dip ride-through capability.
4. If the UR is sensitive to voltage dip, true-off delay timer should be added.
5. Please contact CLP to obtain the recommended LVCOS for reference.

The information and data in this leaflet is purely for reference and shall not form the basis of any decisions as to a particular course of action. Such information or data shall not be applied to any particular set of facts without seeking proper and relevant professional advice. The Company accepts no responsibility for any loss, cost or liability incurred by any person acting or refraining from acting as a result of the information or data contained in this leaflet.